

CSc 21100 - Fundamentals of Computer Systems

Instructor: Prof. Zheng Peng

Project: 02

Name: Kristina Ilyovska

Section: CC1

Date: November 03, 2021

Task 1: Inhibit Gate

The VHDL module implements an Inhibit gate that returns 1 if X input is 1 and Y input is 0. It returns 0 in all other cases.

Entity Declaration


```
entity inhibit_gate is      --also known as "BUT-NOT"
  Port ( x : in  BIT;       --as in x BUT NOT y
        y : in  BIT;
        z : out BIT);
end inhibit_gate;
```

Architecture Definition

```
architecture Inhibit_arch of inhibit_gate is
begin
  z <= '1' when x='1' and y='0' else '0';
end Inhibit_arch;
```

Waveform

The simulation results are as follow:

 

The waveform above covers all test cases. Below is an explanation for each test case in a given ns range.

- [0 ns, 20 ns], Input: x = 0, y = 0; output: z = 0
- [20 ns, 40 ns], Input: x = 0, y = 1; output: z = 0
- [40 ns, 60 ns], Input: x = 1, y = 0; output: z = 1

- The gate works as expected.


The digital circuit detects whether a 4-bit unsigned binary number is prime or not, storing a single bit F as the result.

```
end prime;
```

```
end prime_arch1;
```


Waveform

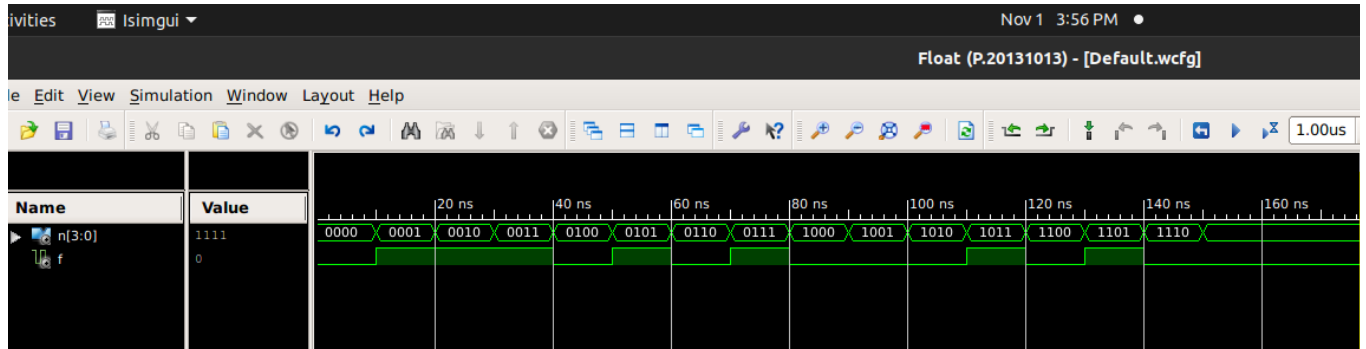The results of the simulation can be seen in the full waveform below:




Here are partial screenshots of the waveform to make it more readable, below each is an explanation of the test cases captured in it:

Pt.1 - First 4 cases

 


- 0: input 0000, output: 0 → 0 is not prime
- 1: input 0001, output: 1 → 1 is prime
- 2: input 0010, output: 1 → 2 is prime
- 3: input 0011, output: 1 → 3 is prime

Pt. 2

 


- 4: input 0100, output: 0 → 4 is not prime
- 5: input 0101, output: 1 → 5 is prime
- 6: input 0110, output: 0 → 6 is not prime
- 7: input 0111, output: 1 → 7 is prime

Pt. 3

 

- 8: input 1000, output: 0 → 8 is not prime
- 9: input 1001, output: 0 → 9 is not prime
- 10: input 1010, output: 0 → 10 is not prime
- 11: input 1011, output: 1 → 11 is prime

Pt. 4

 


- 12: input 1100, output: 0 → 12 is not prime
- 13: input 1101, output: 1 → 13 is prime
- 14: input 1110, output: 0 → 14 is not prime
- 15: input 1111, output: 0 → 115 is not prime (1111 label in screenshot was cut out)

Task 3: Excess-3 Code Detector

The digital circuit detects whether a 4-bit unsigned binary number is valid Excess-3 code word or not. The result is stored in F.

Circuit Diagram

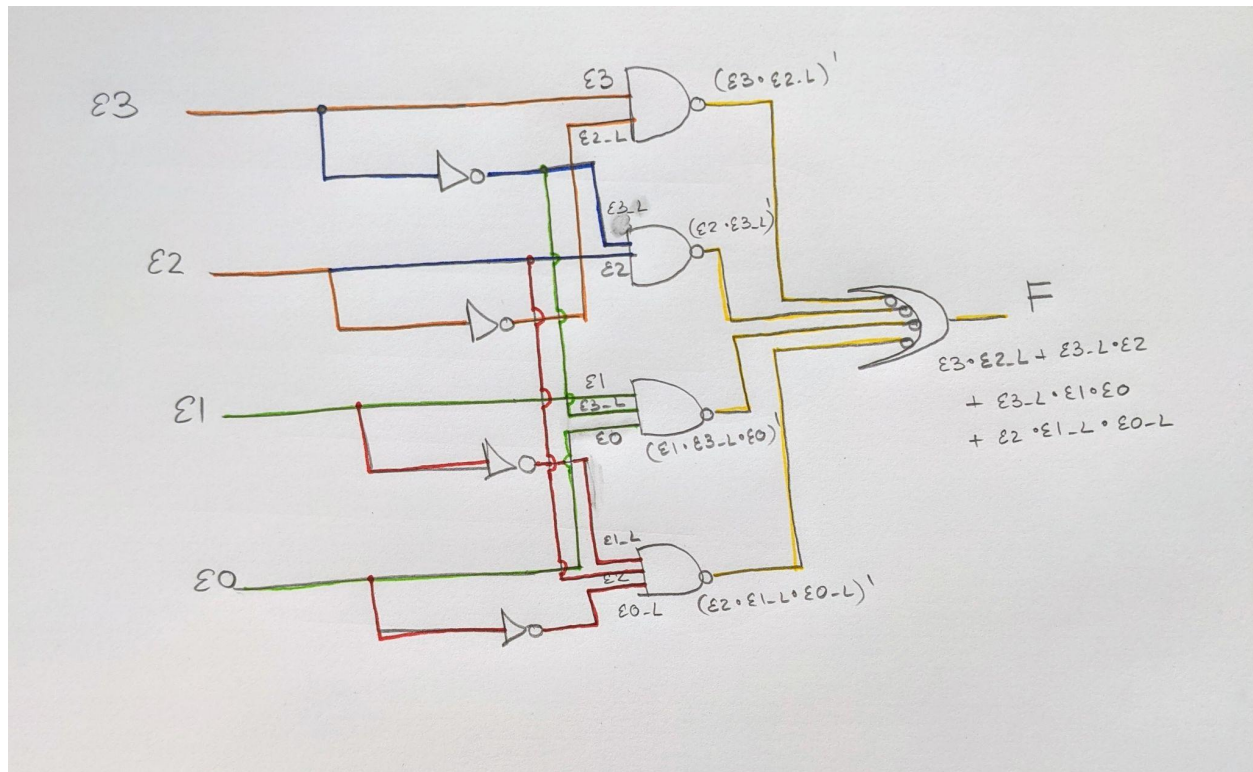

Entity Declaration

```
entity ex3_detector is
    port ( E : in  STD_LOGIC_VECTOR(3 downto 0);  --little endian, MSB first
          F : out STD_LOGIC);
end ex3_detector;
```

Architecture Declaration

```
architecture ex3_detector_arch of ex3_detector is
```

```
    signal E3_L, E2_L, E1_L, E0_L: STD_LOGIC;                                --variables
    signal E3_E2L, E3L_E2, E3L_E1_E0, E2_E1L_E0L: STD_LOGIC;
```

```
    component INV port (I: in STD_LOGIC; O: out STD_LOGIC); end component;    --gates used
    component NAND2 port (I0, I1: in STD_LOGIC; O: out STD_LOGIC); end component;
    component NAND3 port (I0, I1, I2: in STD_LOGIC; O: out STD_LOGIC); end component;
    component NAND4 port (I0, I1, I2, I3: in STD_LOGIC; O: out STD_LOGIC); end component;
```

```
begin
```

```

    U1: INV port map (E(3), E3_L);           --invert E3
    U2: INV port map (E(2), E2_L);           --invert E2
    U3: INV port map (E(1), E1_L);           --invert E1
    U4: INV port map (E(0), E0_L);           --invert E0
    U5: NAND2 port map (E(3), E2_L, E3_E2L); --NAND of 2 inputs
    U6: NAND2 port map (E3_L, E(2), E3L_E2); --NAND of 2 inputs
    U7: NAND3 port map (E3_L, E(1), E(0), E3L_E1_E0); --NAND of 3 inputs
    U8: NAND3 port map (E(2), E1_L, E0_L, E2_E1L_E0L); --NAND of 3 inputs
    U9: NAND4 port map (E3_E2L, E3L_E2, E3L_E1_E0, E2_E1L_E0L, F); --NAND of 4 inputs,
                                                store in F
end ex3_detector_arch;

```

Testbench Program

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY ex3_detector_tb IS
END ex3_detector_tb;

ARCHITECTURE behavior OF ex3_detector_tb IS
    -- Component Declaration for the Unit Under Test (UUT)
    COMPONENT ex3_detector
    PORT(
        E : IN  std_logic_vector(3 downto 0);
        F : OUT std_logic
    );
    END COMPONENT;

    --Inputs
    signal E : std_logic_vector(3 downto 0) := (others => '0');
    --Outputs
    signal F : std_logic;

BEGIN
    -- Instantiate the Unit Under Test (UUT)
    uut: ex3_detector PORT MAP (
        E => E,
        F => F
    );

    -- Stimulus process
    stim_proc: process


```



```
begin
    E <= "0000"; wait for 10 ns;
    E <= "0001"; wait for 10 ns;
    E <= "0010"; wait for 10 ns;
    E <= "0011"; wait for 10 ns;
    E <= "0100"; wait for 10 ns;
    E <= "0101"; wait for 10 ns;
    E <= "0110"; wait for 10 ns;
    E <= "0111"; wait for 10 ns;
    E <= "1000"; wait for 10 ns;
    E <= "1001"; wait for 10 ns;
    E <= "1010"; wait for 10 ns;
    E <= "1011"; wait for 10 ns;
    E <= "1100"; wait for 10 ns;
    E <= "1101"; wait for 10 ns;
    E <= "1110"; wait for 10 ns;
    E <= "1111"; wait for 10 ns;
    wait;
end process;
END;
```


Waveform

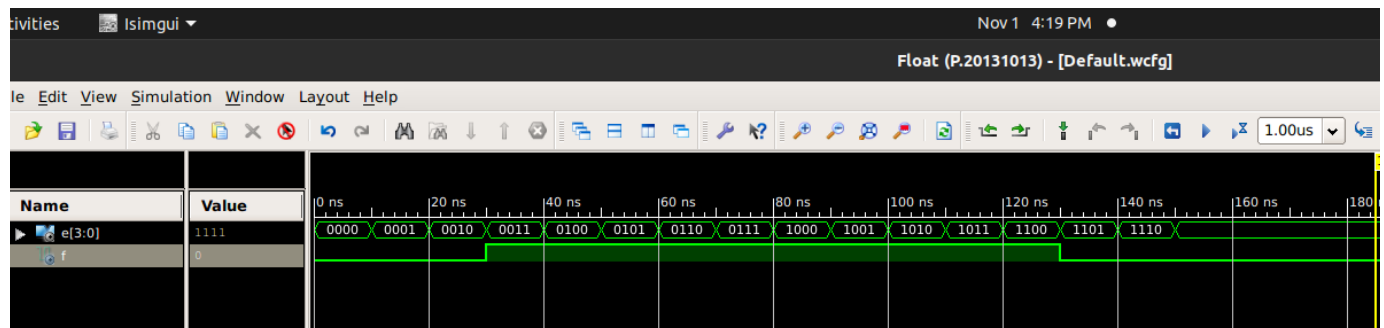The results of the simulation can be seen in the full waveform below:




Here are partial screenshots of the waveform to make it more readable, below each is an explanation of the test cases captured in it:

Pt.1 - First 4 cases

 


- 0: input 0000, output: 0 → 0000 is not valid excess-3 code word
- 1: input 0001, output: 0 → 0001 is not valid excess-3 code word
- 2: input 0010, output: 0 → 0010 is not valid excess-3 code word
- 3: input 0011, output: 1 → 0011 is valid excess-3 code word


Pt. 2

 

 - 4: input 0100, output: 1 → 0100 is valid excess-3 code word
- 5: input 0101, output: 1 → 0101 is valid excess-3 code word
- 6: input 0110, output: 1 → 0110 is valid excess-3 code word
- 7: input 0111, output: 1 → 0111 is valid excess-3 code word



 - 8: input 1000, output: 1 → 1000 is valid excess-3 code word
- 9: input 1001, output: 1 → 1001 is valid excess-3 code word
- 10: input 1010, output: 1 → 1010 is valid excess-3 code word
- 11: input 1011, output: 1 → 1011 is valid excess-3 code word



- 12: input 1100, output: 1 → 1100 is valid excess-3 code word
- 13: input 1101, output: 0 → 1101 is not valid excess-3 code word
- 14: input 1110, output: 0 → 1110 is not valid excess-3 code word
- 15: input 1111, output: 0 → 1111 is not valid excess-3 code word